

NAME:

ID:



ECE 210 Circuits
Fall 2014 Quiz 2 November 3, 2014
Instructor: Prof. M. Shridhar

Please sign and observe Honor Code

I did not receive or give unauthorized help in this quiz.

STUDENT ID:

M. Shridhar

NAME:



Signature

Answer all questions. Write your answer in the space provided below the question. Use the **FACING** side to continue your answers. All rough work should be turned in. Partial credit is given if all steps are clearly described.

NOTE: THIS QUIZ TESTS YOU ON YOUR ABILITY TO ANALYZE AC AND DC LINEAR CIRCUITS, USING NETWORK REDUCTION, AND NODAL ANALYSIS.

NAME:

ID:

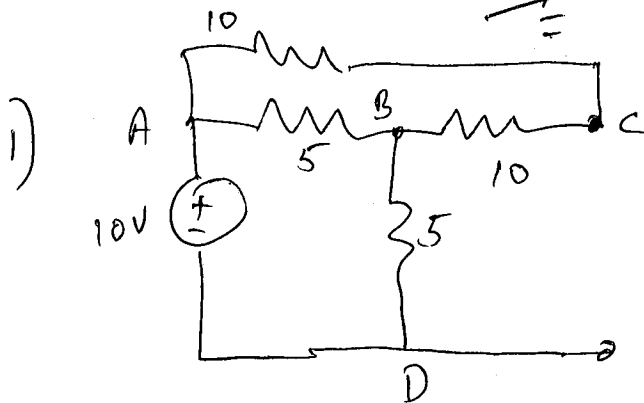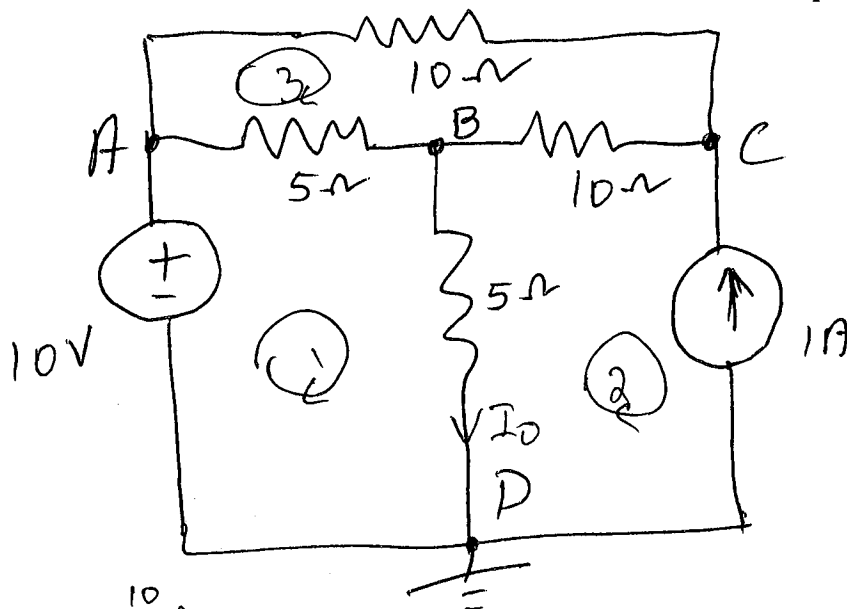
1. Using superposition find the current I_0 . Show all the steps.

$$B: \left(\frac{1}{5} + \frac{1}{5} + \frac{1}{10} \right) V_B - \frac{1}{10} V_C = 2 \Rightarrow 5V_B - V_C = 20$$

$$C: -\frac{1}{10} V_B + \left(\frac{1}{10} + \frac{1}{10} \right) V_C = 1 \Rightarrow -V_B + 2V_C = 10$$

$$\begin{array}{r} 10V_B - 2V_C = 40 \\ 9V_B = 50 \Rightarrow V_B = \frac{50}{9} \end{array}$$

$$I_{01} = \frac{10}{9} A$$

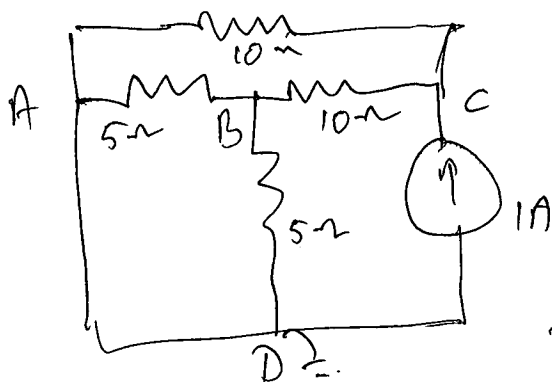

$$V_A = 0$$

$$B: \left(\frac{1}{5} + \frac{1}{5} + \frac{1}{10} \right) V_B - \frac{1}{10} V_C = 0 \Rightarrow 5V_B - V_C = 0$$

$$C: -\frac{1}{10} V_B + \left(\frac{1}{10} + \frac{1}{10} \right) V_C = 1 \Rightarrow -V_B + 2V_C = 10$$

$$\begin{array}{r} 10V_B - 2V_C = 0 \\ 9V_B = 10 \\ V_B = \frac{10}{9} \end{array}$$

$$I_{02} = \frac{2}{9}$$

$$I_0 = \frac{10}{9} + \frac{2}{9} = \frac{12}{9} = \frac{4}{3} A$$

(2)

2. Write node and loop equations that will allow you to find V_B and V_C . Show all steps clearly and legibly. Find V_B and V_C using one of the two methods. Use the circuit of Q1.

$$B: \left(\frac{1}{5} + \frac{1}{5} + \frac{1}{10}\right)V_B - \frac{1}{10}V_C = \frac{10}{5} \Rightarrow \underline{5V_B - V_C = 20}$$

$$C: -\frac{1}{10}V_B + \left(\frac{1}{10} + \frac{1}{10}\right)V_C = \frac{10}{10} + 1$$

$$-V_B + 2V_C = 20$$

$$10V_B - 2V_C = 40$$

$$9V_B = 60 \Rightarrow V_B = \frac{60}{9} = \frac{20}{3}$$

$$V_C = 5V_B - 20$$

$$\frac{100}{3} - \frac{60}{3} = \frac{40}{3} \checkmark$$

$$V_B = \frac{20}{3} \text{ V}$$

$$V_C = \frac{40}{3} \checkmark$$

$$\underline{\text{Loop}} \quad I_2 = -1 \text{ A}$$

$$\underline{\text{Loop 1}}: 10I_1 - 5I_2 - 5I_3 = 10 \Rightarrow 10I_1 - 5I_3 = 5$$

$$\underline{\text{Loop 2}}: -5I_1 - 10I_2 + 25I_3 = 0 \Rightarrow -5I_1 + 25I_3 = -10$$

$$-10I_1 + 50I_3 = -20$$

$$45I_3 = -15 \Rightarrow I_3 = -\frac{1}{3}$$

$$10I_1 = 5 + 5I_3 = 5 - \frac{5}{3} = \frac{10}{3}$$

$$I_1 = \frac{1}{3} \text{ A}$$

$$V_B = 5(I_1 - I_2) = 5\left(\frac{1}{3} + 1\right) = 5 \cdot \frac{4}{3} = \underline{\underline{\frac{20}{3} \text{ V}}}$$

$$V_C = 5(I_1 - I_2) + 10(I_3 - I_2) = 5I_1 - 15I_2 + 10I_3$$

$$5/3 + 15 - \frac{10}{3} = \underline{\underline{\frac{40}{3} \text{ V}}}$$

$$I_0 = \frac{V_B}{5} = \frac{20}{15} = \underline{\underline{\frac{4}{3} \text{ A}}}$$


NAME:

ID:

NAME:

ID:

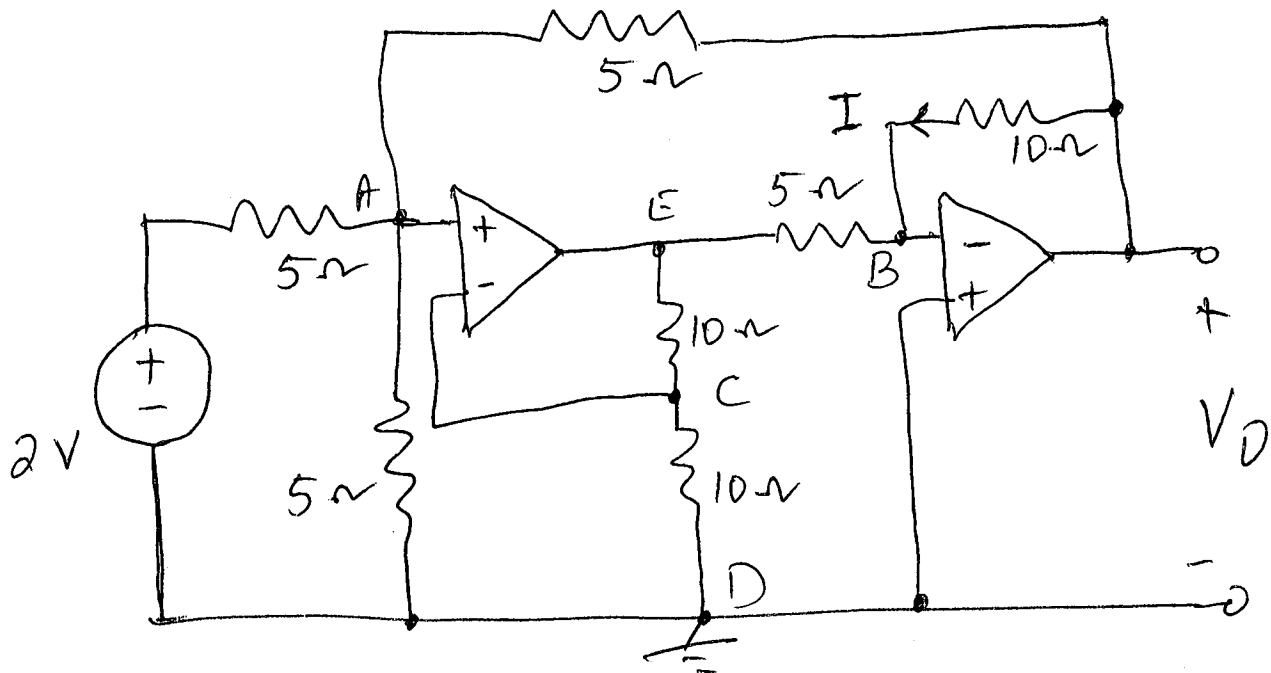3. Find the current I in the circuit shown below. Show all steps clearly.



$$V_A = V_C = \frac{V_E}{2}$$

$$V_B = 0$$

$$A: \frac{V_A - 2}{5} + \frac{V_A}{5} + \frac{V_A - V_D}{5} = 0$$

$$\left(\frac{1}{5} + \frac{1}{5} + \frac{1}{5}\right)V_A - \frac{1}{5}V_D = \frac{2}{5}$$

$$3V_A - V_D = 2$$

$$B: \frac{V_B - V_E}{5} + \frac{V_B - V_D}{10} = 0$$

$$\frac{V_E - V_D}{10} = 0 \quad \frac{V_D}{10} = \frac{V_E}{5}, \quad V_D = -2V_E$$

$$V_D = -2V_E, \quad V_A = \frac{V_E}{2} = -\frac{1}{4}V_D$$


$$\rightarrow V_E = -\frac{1}{2}V_D$$

$$-\frac{3}{4}V_D - V_D = 2$$

$$-\frac{7}{4}V_D = 2$$

$$V_D = -\frac{8}{7}V = -\frac{8}{7}V \quad (5)$$

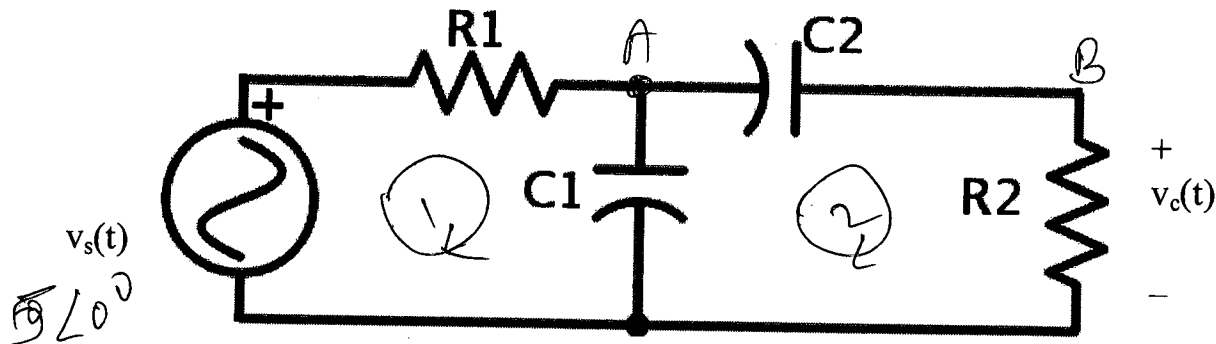4. Find $v_c(t)$ for the circuit shown below. How many ways can you solve this problem. List them. Choose one method, write the equations and find $v_c(t)$. Show all the steps.



$$R1 = 2\Omega, R2 = 4\Omega, C1 = 0.5F, C2 = 0.25F$$

$$v_s(t) = 5 \cos(t), \quad \omega = 1 \text{ rad/s}$$

$$C1 = 0.5F \rightarrow \frac{1}{j\omega C} = \frac{-j}{0.5} = -j2$$

$$C2 = 0.25F \rightarrow \frac{1}{j\omega C} = \frac{-j}{0.25} = -j4$$

1) Loop

2) Node

3) Network reduction

$$\text{Loop 1: } R1 + (-j2)I_1 + j2I_2 = 5\angle 0^\circ$$

$$\text{Loop 2: } (4 - j6)I_2 + j2I_1 = 0$$

$$\text{Node A: } \left(\frac{1}{-j2} + \frac{1}{2} + \frac{1}{-j4} \right) V_A - \frac{1}{-j4} V_B = \frac{5\angle 0^\circ}{2}$$

$$B: -\frac{1}{-j4} V_A + \left(\frac{1}{4} + \frac{1}{-j4} \right) V_B = 0$$

(6)

NAME:

ID: