
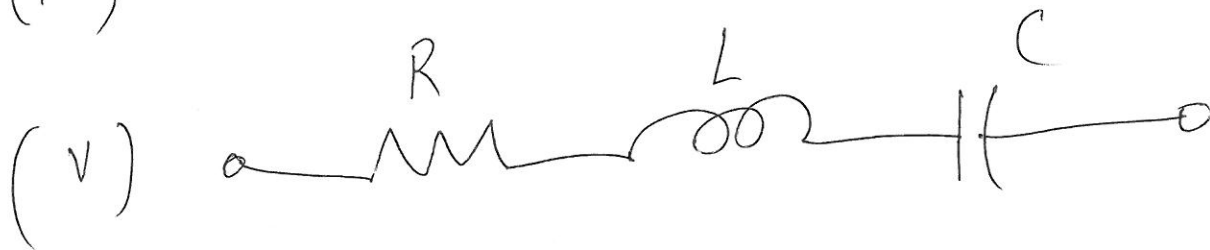
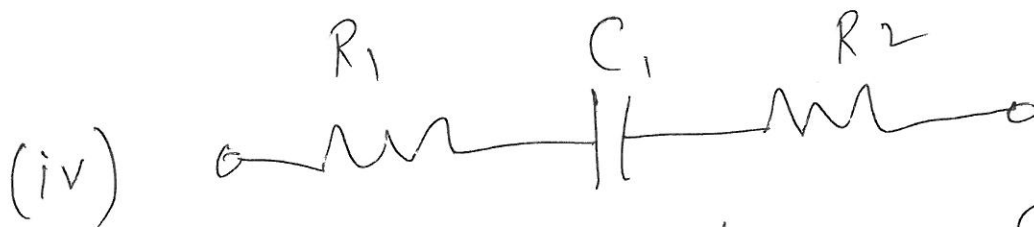
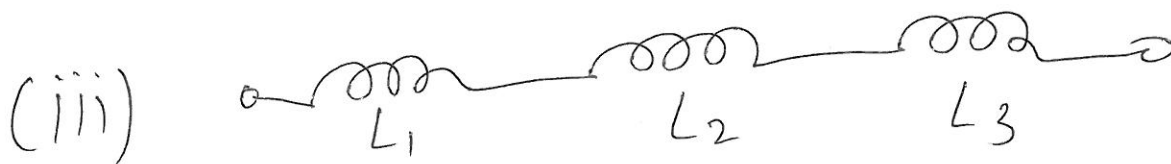
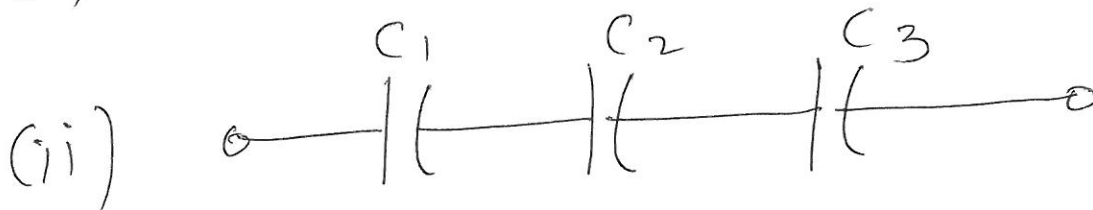


Series and Parallel Combinations


①

Examples :

a) Series Connections

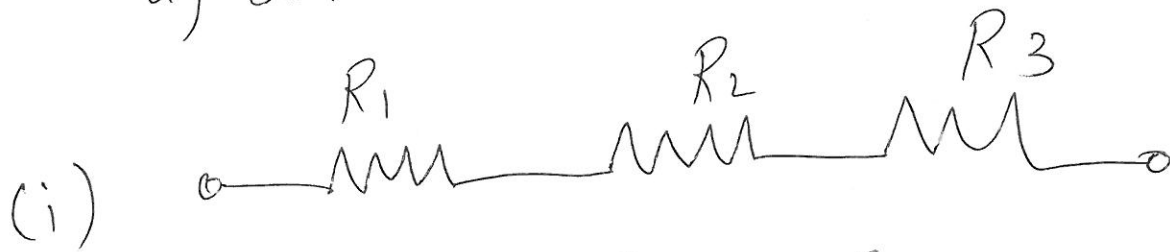


(i)

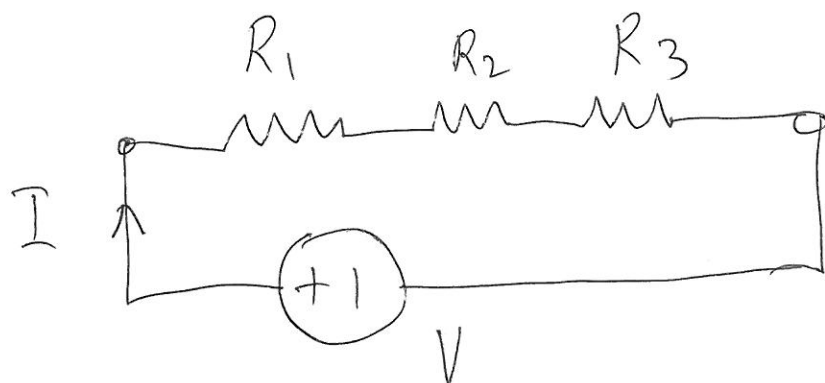

Using KVL we can show

$$(R_1 + R_2 + R_3)I = V$$

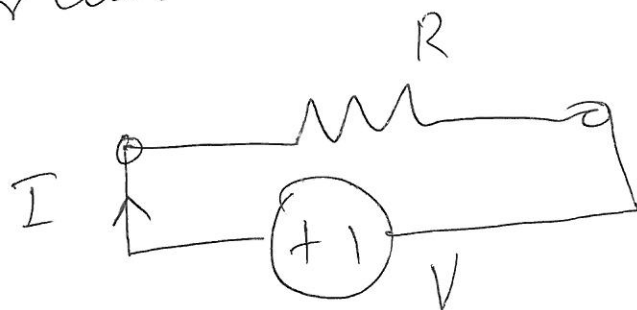Then we can derive an equivalent circuit as shown below




$$RI = V$$

If we have the same I in both circuits then we can show that

$$R = R_1 + R_2 + R_3$$

ie Resistors in series add

(ii)

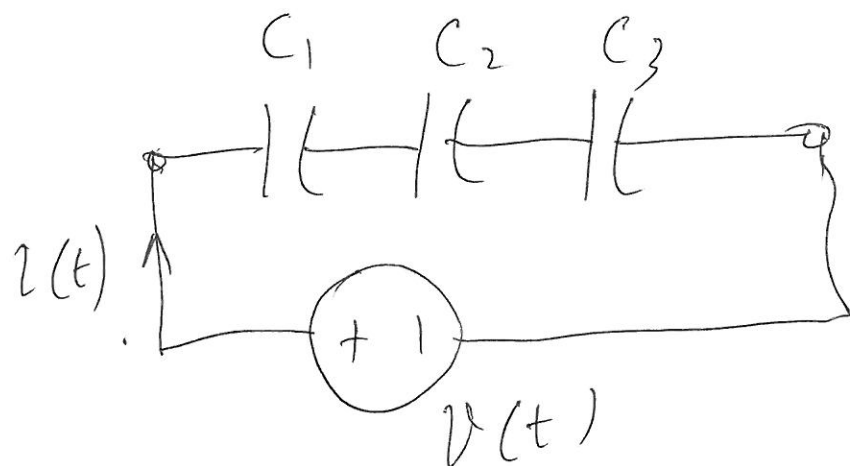


3

Using KVL we can write

$$v(t) = \frac{1}{C_1} \int i(t) dt + \frac{1}{C_2} \int i(t) dt + \frac{1}{C_3} \int i(t) dt \quad - (1)$$

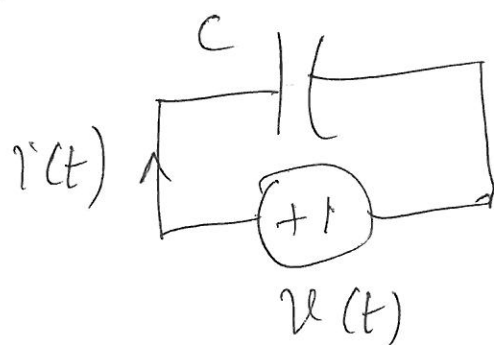We will construct a circuit with one capacitor that will have the same current as the circuit with three capacitors




$$v(t) = \frac{1}{C} \int i(t) dt \quad - (2)$$

This leads to $\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$

Capacitors in series add reciprocally

(iii)

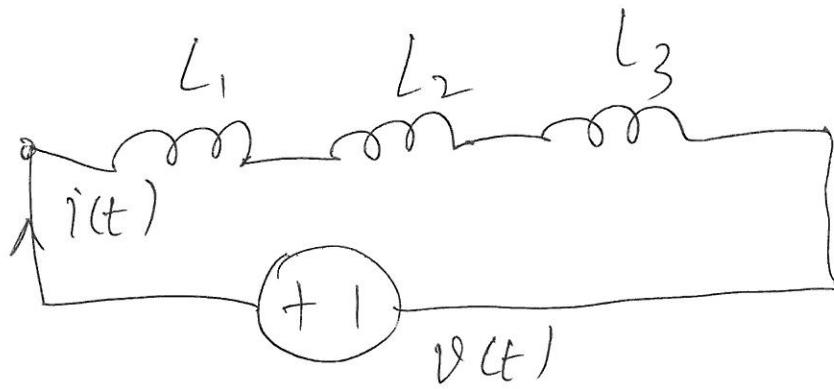


(4)

Using KVL we can write

$$v(t) = L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + L_3 \frac{di}{dt}$$
$$= (L_1 + L_2 + L_3) \frac{di}{dt}$$

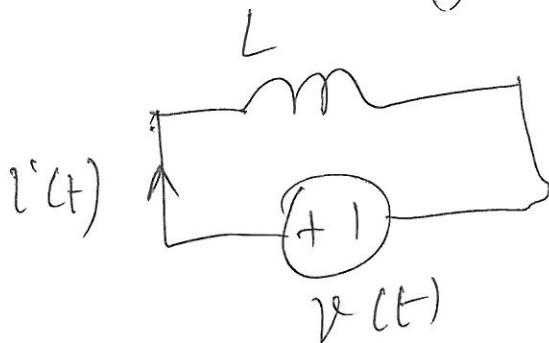We can construct an equivalent circuit with one inductor L that will have the same voltage and current



$$v(t) = L \frac{di}{dt}$$

This leads to $L = L_1 + L_2 + L_3$

Inductors in series add

(5)

(iv)

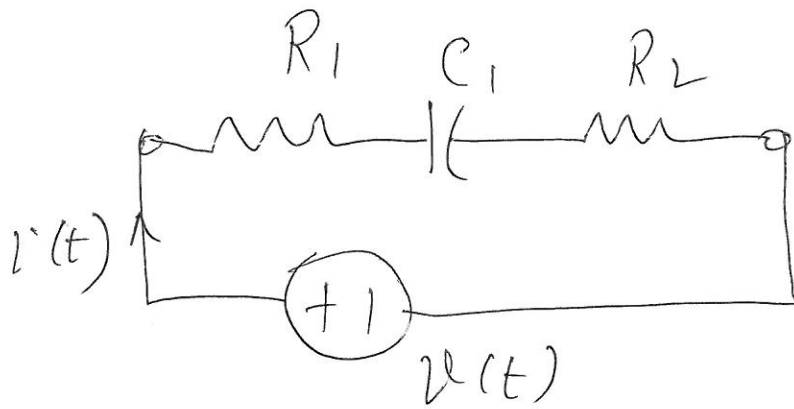


Fig 1

This is a special circuit and we will handle it in two ways

a) $v(t)$ is an arbitrary time function

$$\begin{aligned} \text{Then } v(t) &= R_1 i(t) + \frac{1}{C_1} \int i(t) dt + R_2 i(t) \\ &= \left(R_1 + R_2 + \frac{1}{C_1 D} \right) i(t) \end{aligned}$$

Note: $\frac{1}{D}$ is the integral operator

b) $v(t) = A e^{j\omega_0 t}$ — AC circuit

In this case we can replace the capacitor with its impedance $\frac{1}{j\omega_0 C}$. We redraw

the circuit as shown in Fig 2

(6)

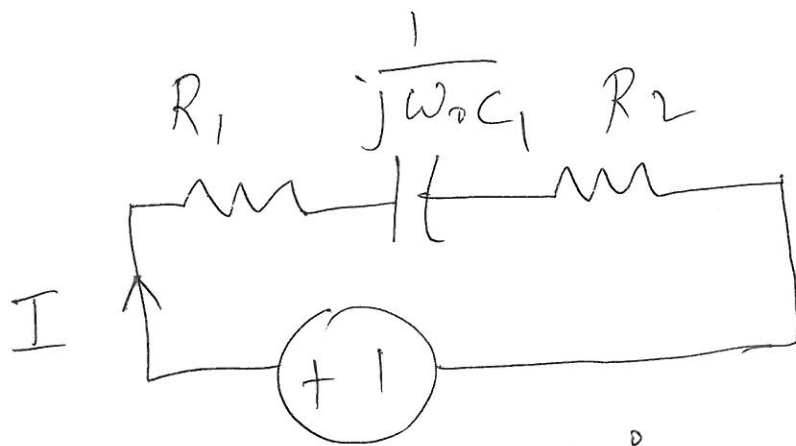


Fig 2

$$V = A \angle 0^\circ$$

We now explain this. $A e^{j(\omega_0 t + \theta)}$ is a complex sinusoidal signal with amplitude A and initial angle θ . In Fig 2, this angle is 0° i.e. $\theta = 0^\circ$.

~~where~~ V and I are phasor

representations of voltage and current when we deal with an AC circuit we simply write the KVL equation as

$$\begin{aligned} V &= R_1 I + \frac{1}{j\omega_0 C_1} I + R_2 I \\ &= \left(R_1 + \frac{1}{j\omega_0 C_1} + R_2 \right) I \end{aligned}$$


We can write this as

$$V = Z I \quad \text{where}$$

$$Z = R_1 + R_2 + \frac{1}{j\omega_0 C}$$

Z is called the impedance of the circuit. In this series combination we can say that

Impedances in Series add

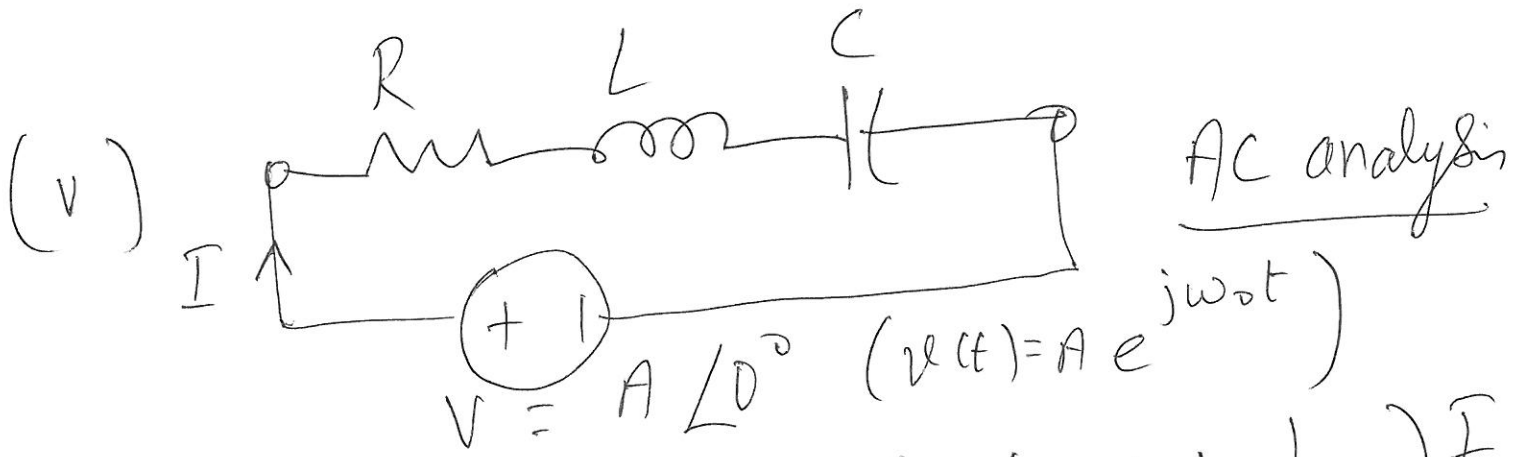

Using KVL, $V = (R + j\omega_0 L + \frac{1}{j\omega_0 C}) I$


$$V = Z I, \quad Z = R + j\omega_0 L + \frac{1}{j\omega_0 C}$$

Impedances in Series add

Parallel Combinations

8

(i)

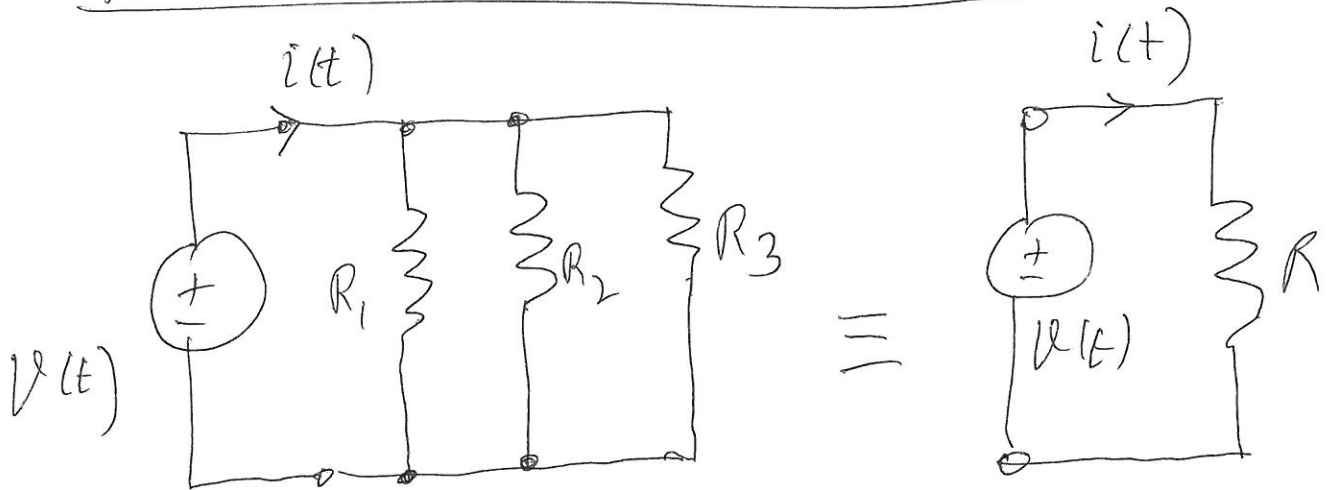

using KCL we can write

$$i(t) = \frac{v(t)}{R_1} + \frac{v(t)}{R_2} + \frac{v(t)}{R_3} = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) v(t)$$

For the circuit on the right we get



$$i(t) = \frac{v(t)}{R}$$

If $v(t)$ and $i(t)$ are the same in both circuits then we can show that

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

Resistors in parallel add reciprocally

(ii)

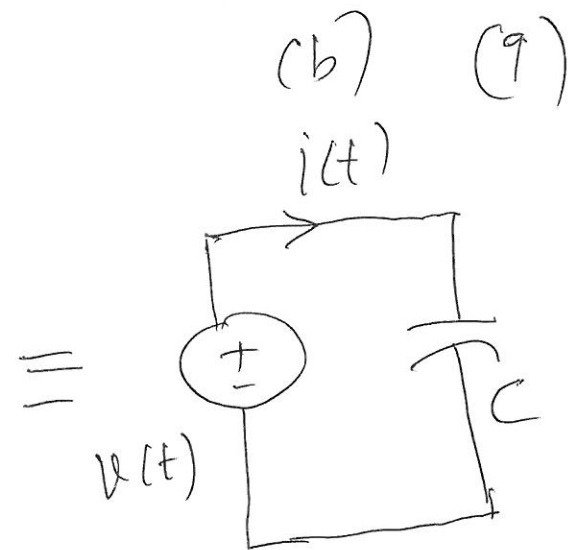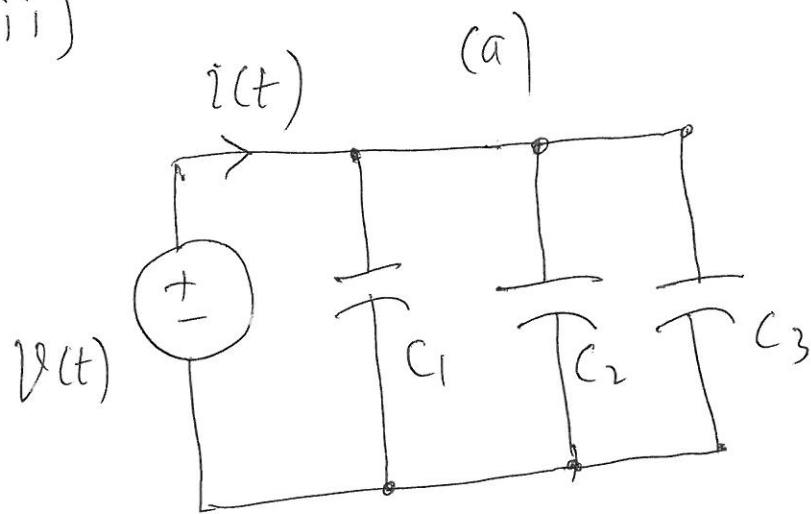

Using KCL we can write for both circuits



$$i(t) \quad \text{for (a)} = C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt} + C_3 \frac{dv}{dt}$$

$$i(t) \quad \text{for (b)} = C \frac{dv}{dt}$$

If $i(t)$ and $v(t)$ are the same in both circuits then we can establish the following relationship:

$$C = C_1 + C_2 + C_3$$

ie Capacitors in parallel add

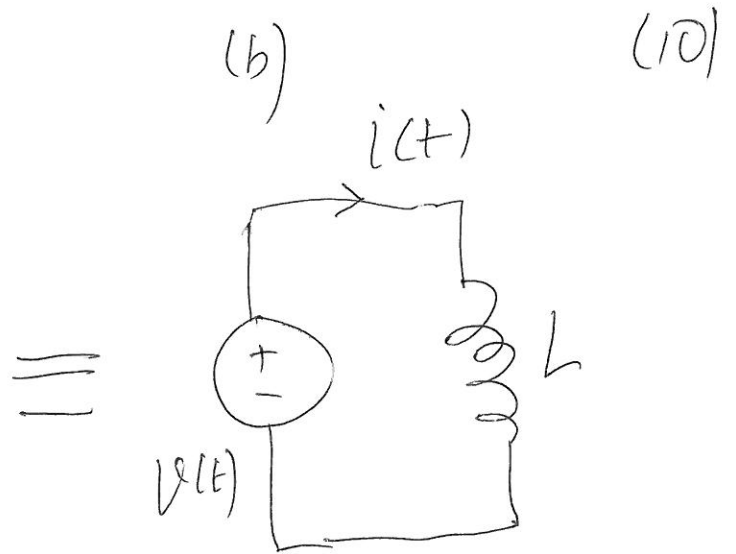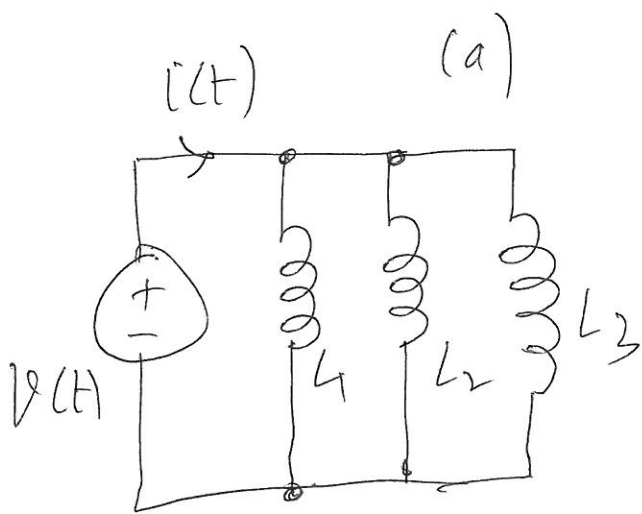

using KCL we get

$$i(t) = \frac{1}{L_1} \int v(t) dt + \frac{1}{L_2} \int v(t) dt + \frac{1}{L_3} \int v(t) dt$$

$$= \left(\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} \right) \int v(t) dt \rightarrow (a)$$

$$i(t) = \frac{1}{L} \int v(t) dt \rightarrow (b)$$


If $v(t)$ and $i(t)$ are the same for both circuits then we can show that

$$\frac{1}{L} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$$

Inductors in parallel add reciprocally


Special Case - AC Circuits

(11)

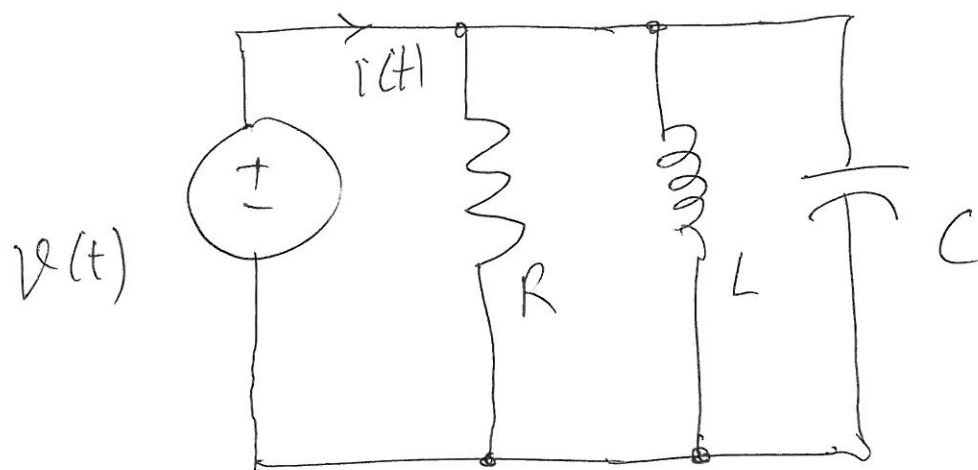

For AC Circuits $v(t) = A e^{j(\omega_0 t)}$

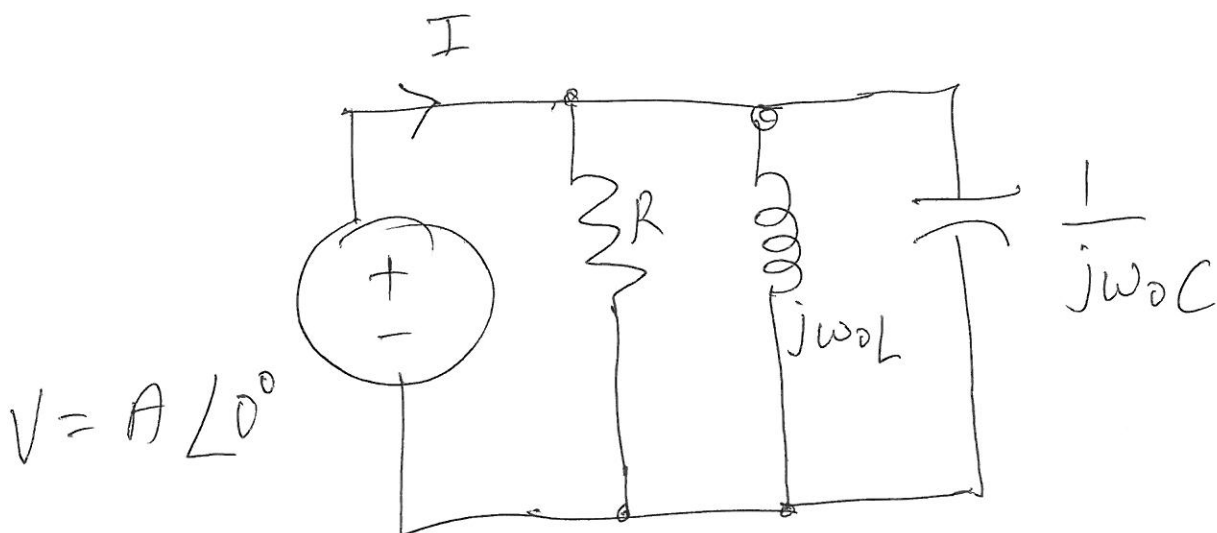When $v(t)$ is an AC signal we ~~write~~ redraw the circuit




KCL: $I = \left(\frac{1}{R} + \frac{1}{j\omega_0 L} + j\omega_0 C \right) V$


ie impedances in parallel add reciprocally

Practice problem 1


(12)

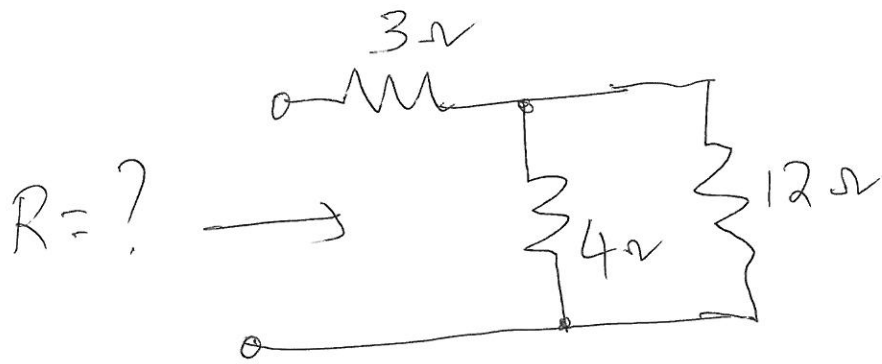

(a)

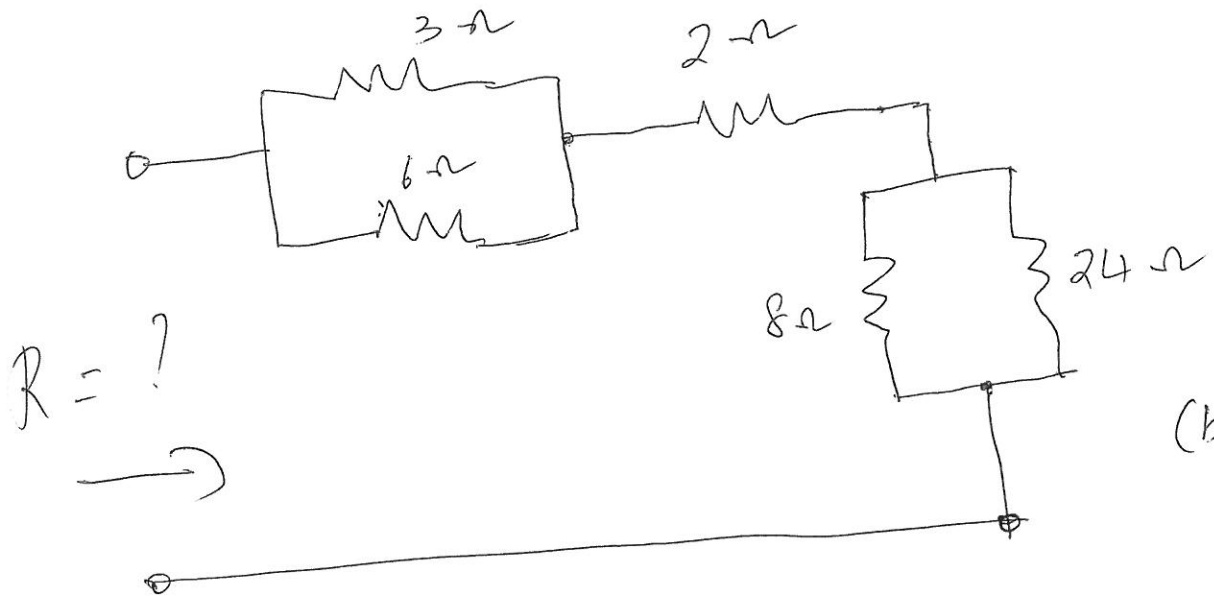

(b)

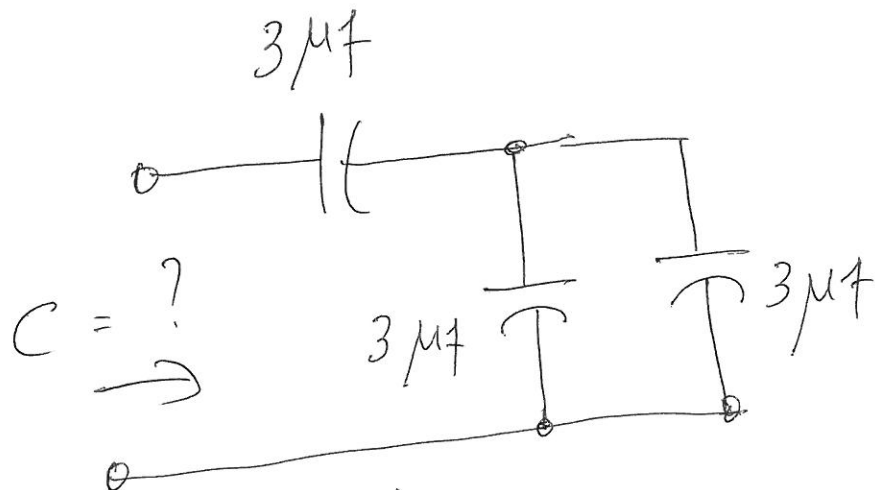

(c)

