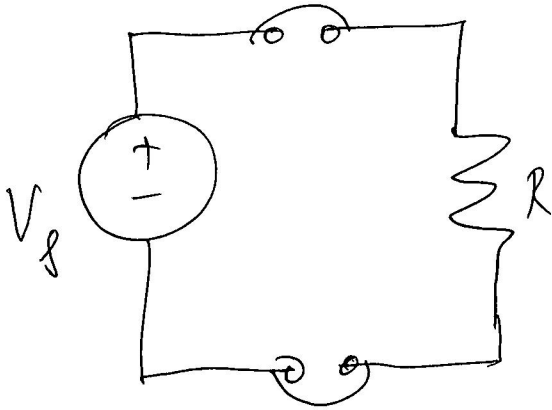



Voltage and Current Sources

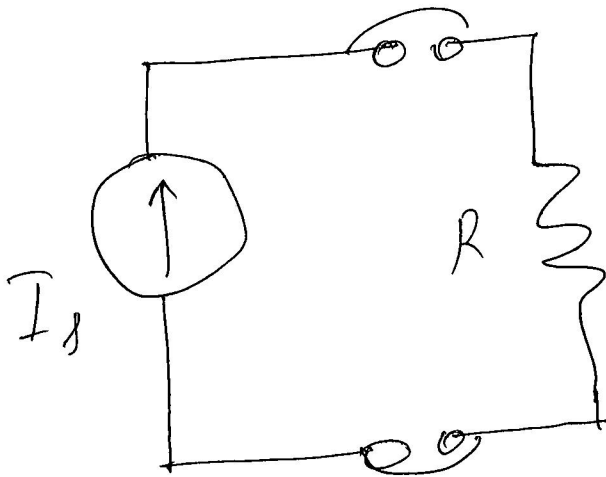(1)

Ideal Sources





V_s is the voltage across R no matter what the value of R is



I_s will be the current thro' R no matter what R is

Practical Sources

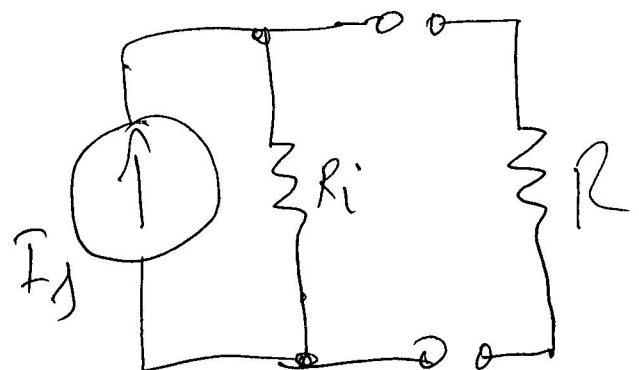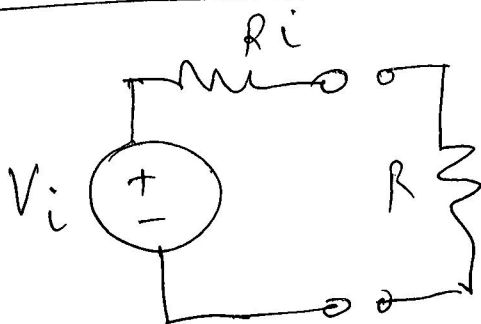


(2)

In a practical voltage source, the voltage across R will vary depending on the value of R

Similarly, The current thro' R will vary depending on what its value is

Controlled Source

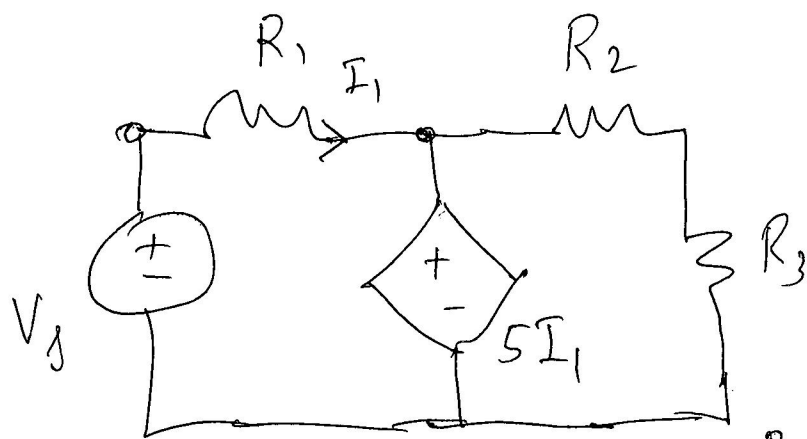

In this circuit



represents a

Controlled voltage source and its value


is $5I_1$, where I_1 is the current thro' R_1

(3)


We call this ~~CCVS~~ CCVS which stands for Current Controlled Voltage Source.

Other examples

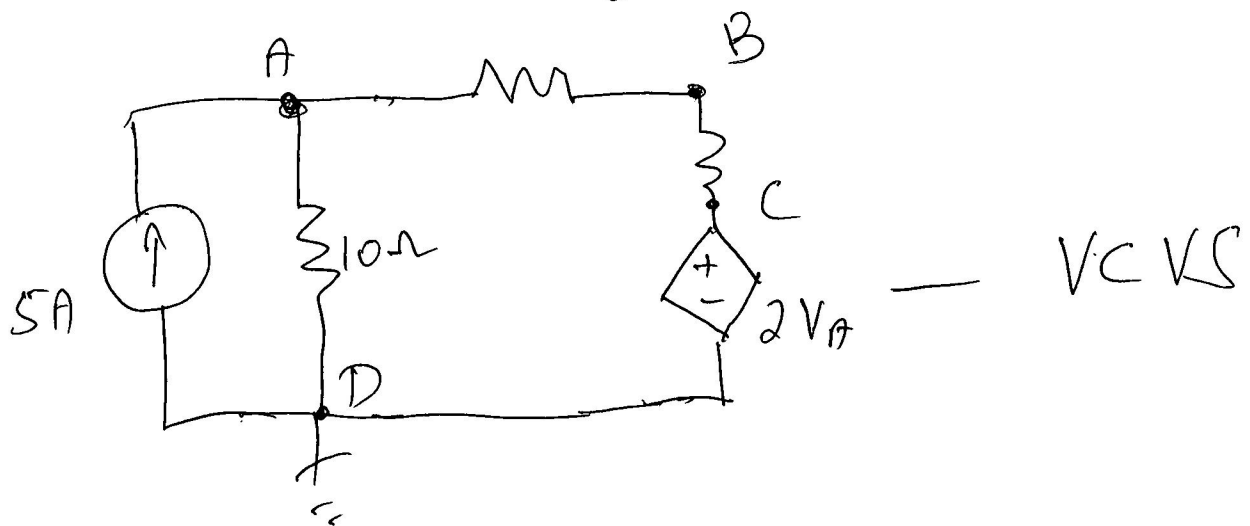
1) VCVS - voltage Controlled Voltage Source



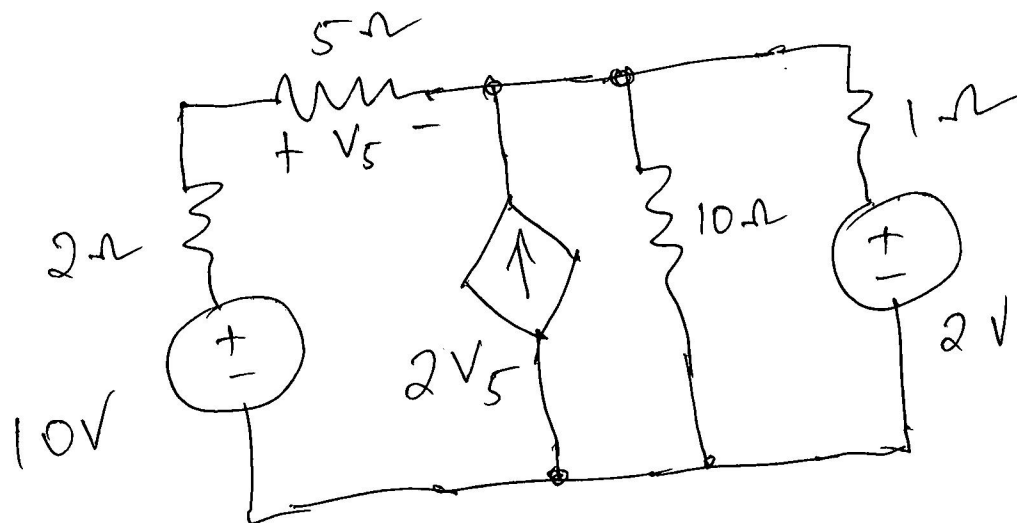2) VCCS - voltage Controlled Current Source




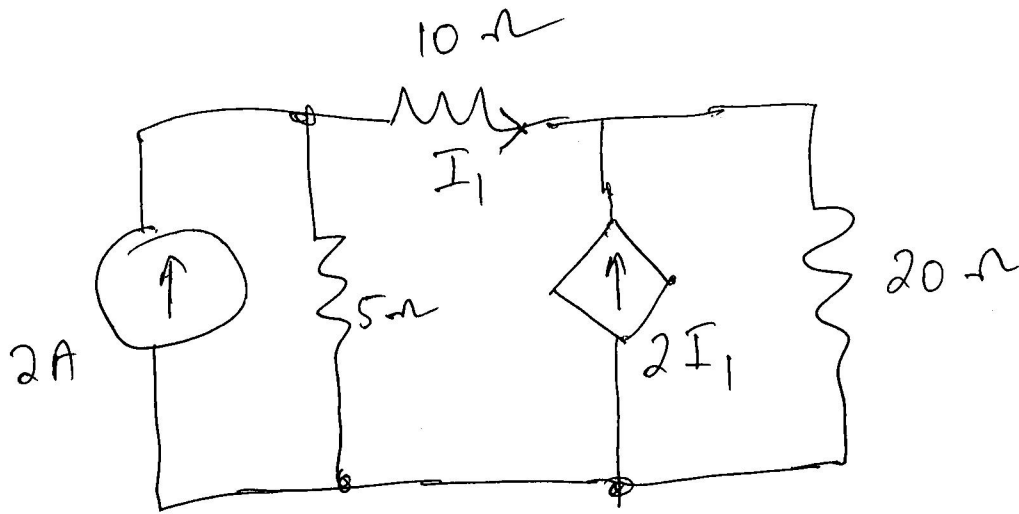3) CCCS - Current Controlled Current Source (4)



Examples




Find I_o for the circuit shown below

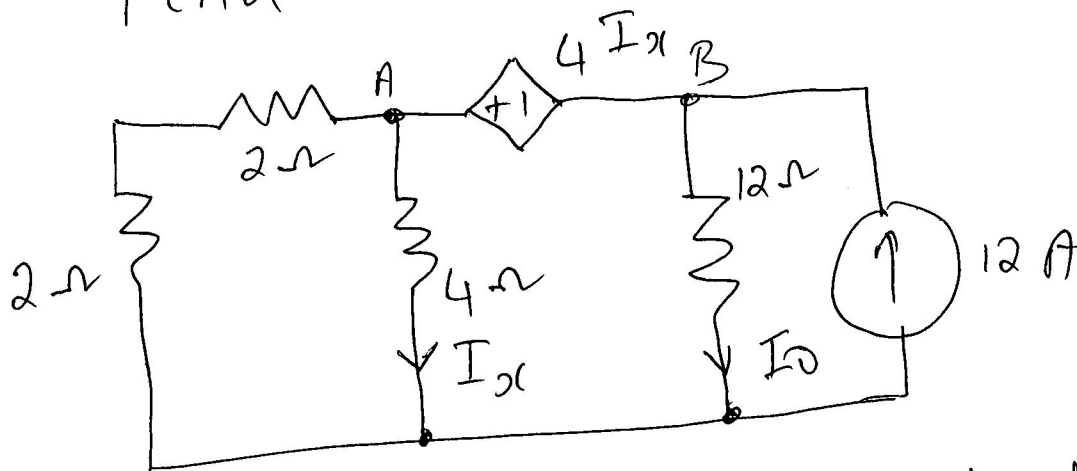

This problem can be solved by manipulating the circuit.

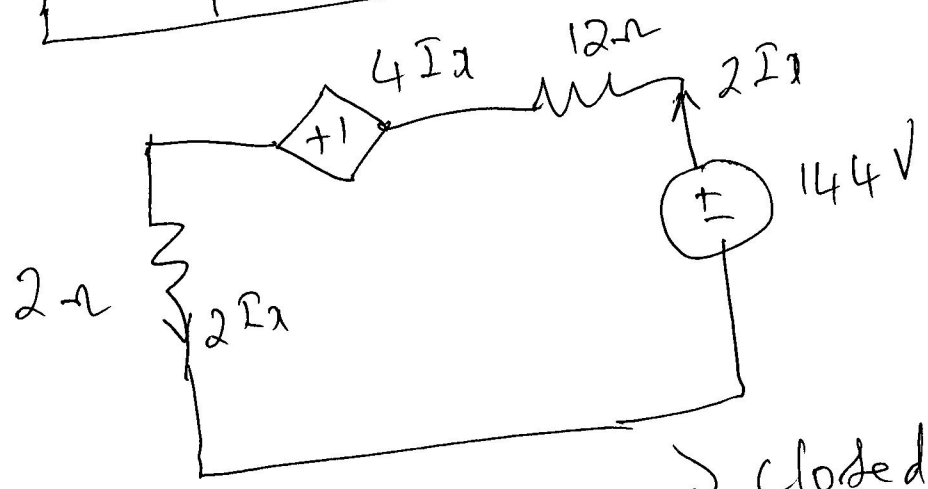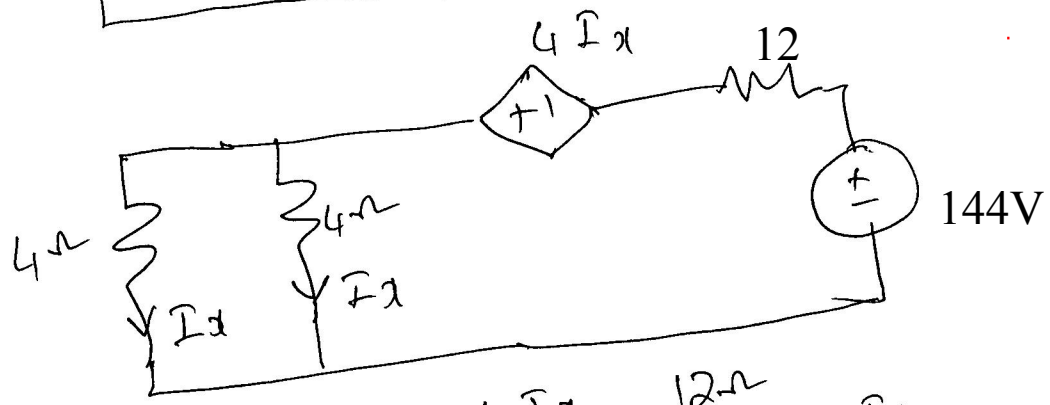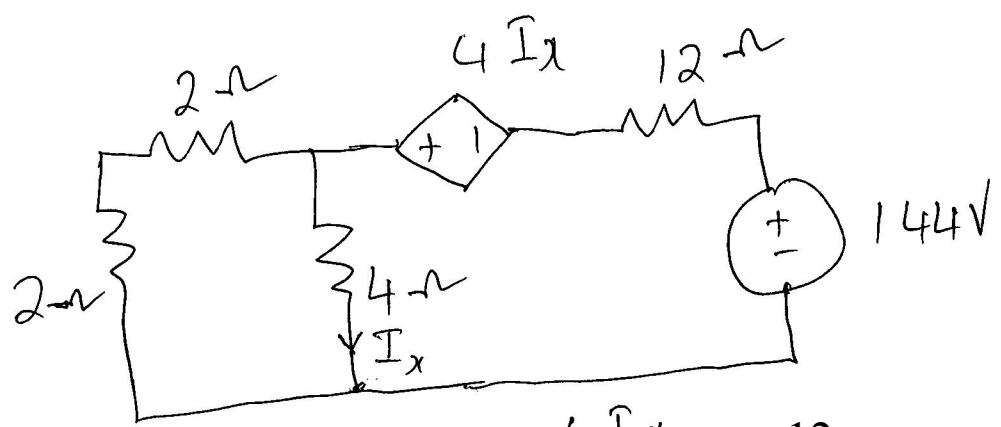(5)

Using Source Conversion we can redraw the circuit as



KVL says voltage around closed path add up to zero

$$4I_x - 24I_x + 144V - 4I_x = 0$$

$$24I_x = 144, \quad I_x = 6A$$

If $I_x = 6A$, then at node B in the original circuit, we apply KCL

~~$$2I_x + I_o - 12 = 0$$~~

$$2I_x + I_o - 12 = 0$$

$$I_o = 12 - 2I_x = 12 - 12 = 0$$

$I_o = 0A$